
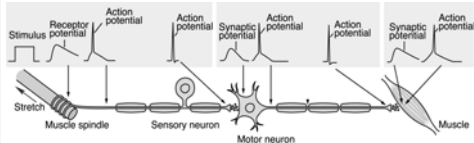


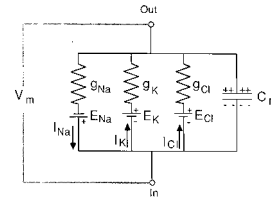Generator Potentials, Synaptic Potentials and Action Potentials All Can Be Described by the Equivalent Circuit Model of the Membrane



PNS, Fig 2-11

Equivalent Circuit Model of the Neuron




The Nerve (or Muscle) Cell can be Represented by a Collection of Batteries, Resistors and Capacitors


Equivalent Circuit of the Membrane and Passive Electrical Properties

- Equivalent Circuit of the Membrane
 - What Gives Rise to C, R, and V?
 - Model of the Resting Membrane
- Passive Electrical Properties
 - Time Constant and Length Constant
 - Effects on Synaptic Integration
- Voltage-Clamp Analysis of the Action Potential

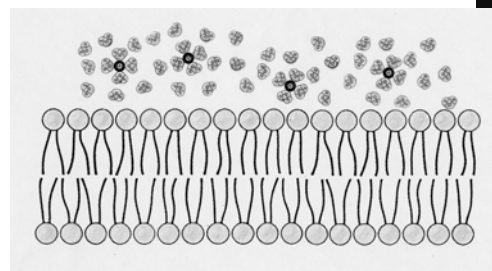Ions Cannot Diffuse Across the Hydrophobic Barrier of the Lipid Bilayer



The Lipid Bilayer Acts Like a Capacitor

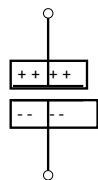








$$V_m = Q/C$$

$$\Delta V_m = \Delta Q/C$$


ΔQ must change before ΔV_m can change

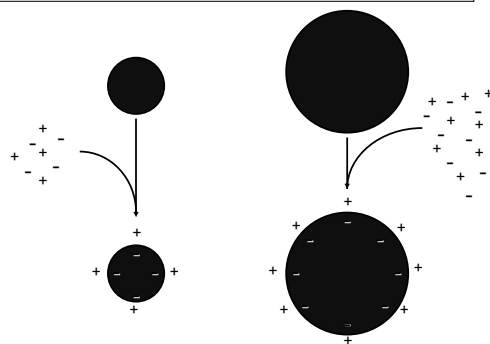Capacitance is Proportional to Membrane Area



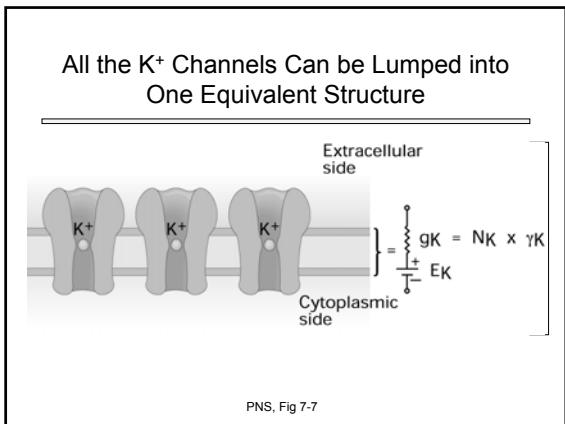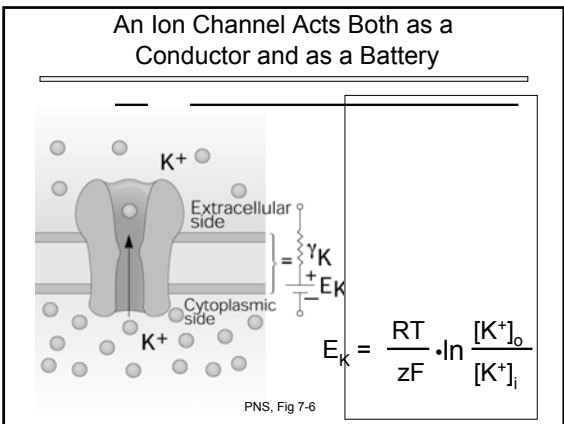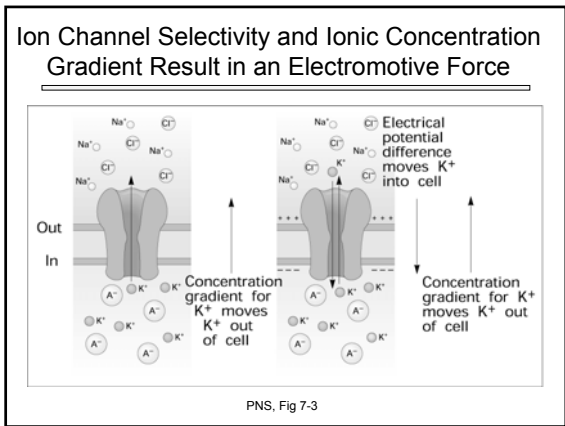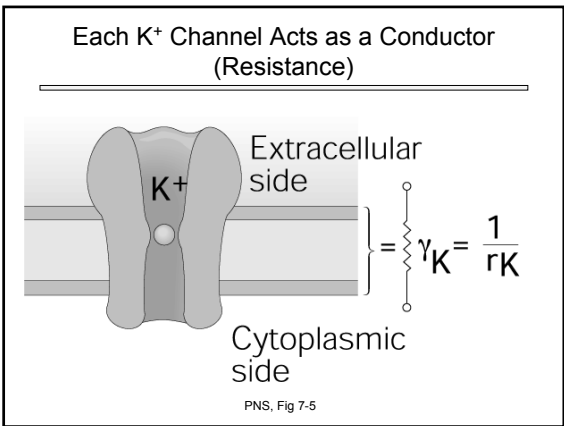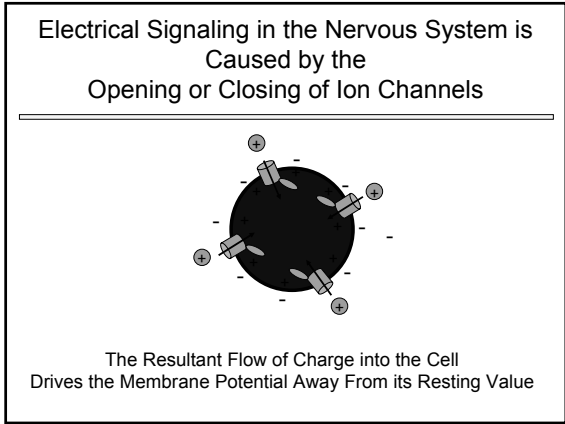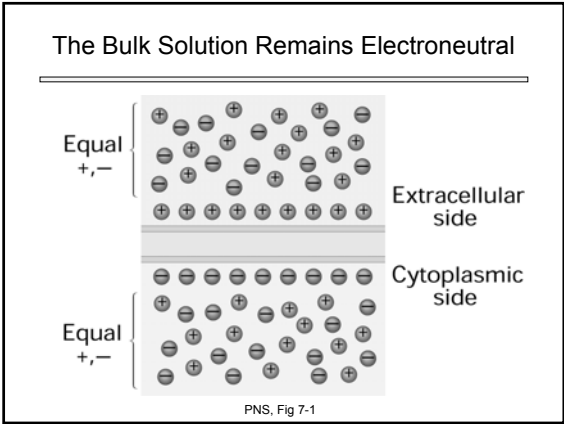


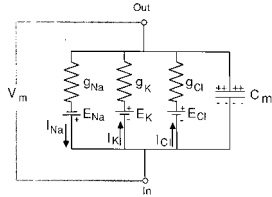An Ionic Battery Contributes to V_m in Proportion to the Membrane Conductance for That Ion




$$V_m = \frac{g_K \cdot E_K + g_{Cl} \cdot E_{Cl} + g_{Na} \cdot E_{Na}}{g_K + g_{Cl} + g_{Na}}$$

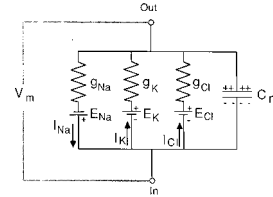When g_K is Very High, $g_K \cdot E_K$ Predominates




$$V_m = \frac{g_K \cdot E_K + \cancel{g_{Cl} \cdot E_{Cl}} + \cancel{g_{Na} \cdot E_{Na}}}{g_K + \cancel{g_{Cl}} + \cancel{g_{Na}}}$$

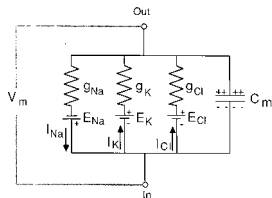The K^+ Battery Predominates at Resting Potential




$$V_m \approx \frac{g_K \cdot E_K}{g_K} \quad \boxed{}$$

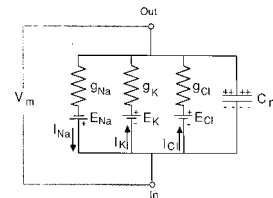The K^+ Battery Predominates at Resting Potential



$$V_m \approx \frac{\cancel{g_K} \cdot E_K}{\cancel{g_K}} \quad \boxed{}$$


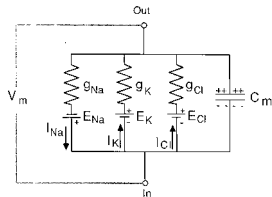
This Equation is Qualitatively Similar to the Goldman Equation






$$V_m = \frac{g_K \cdot E_K + g_{Cl} \cdot E_{Cl} + g_{Na} \cdot E_{Na}}{g_K + g_{Cl} + g_{Na}}$$







The Goldman Equation




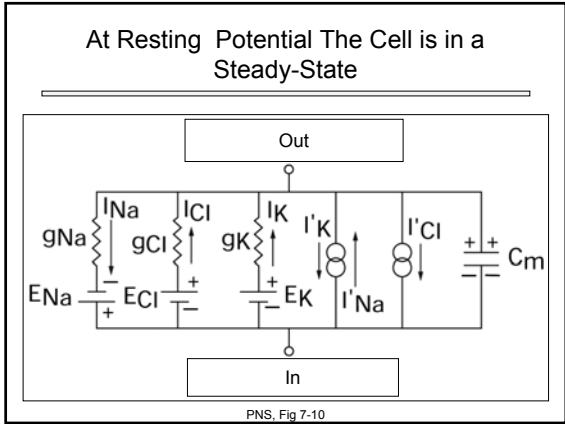
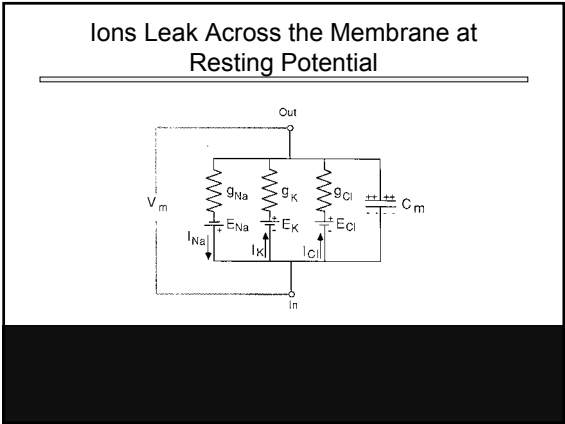
$$\frac{RT}{zF} \ln \frac{(P_K \{K^+\}_o + P_{Na} \{Na^+\}_o + P_{Cl} \{Cl^-\}_i)}{(P_K \{K^+\}_i + P_{Na} \{Na^+\}_i + P_{Cl} \{Cl^-\}_o)}$$






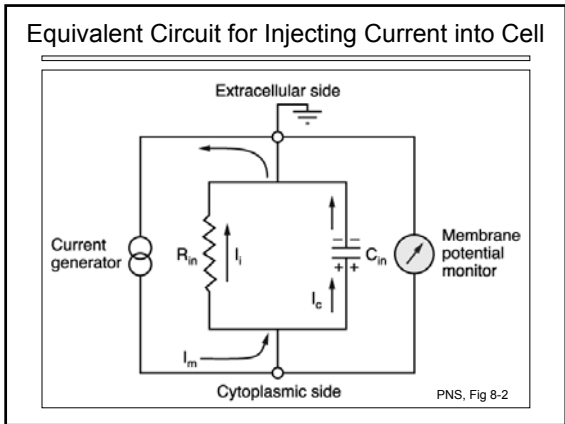
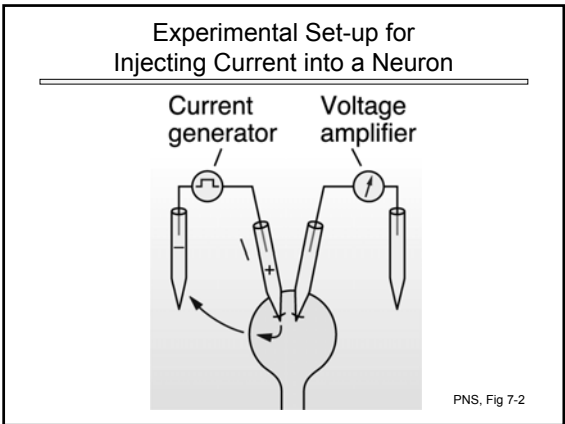
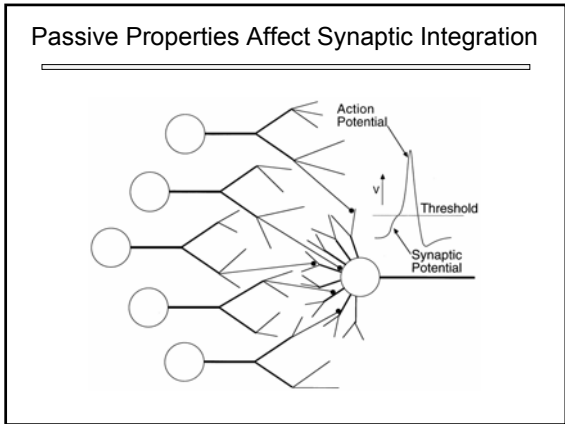
- ### Equivalent Circuit of the Membrane and Passive Electrical Properties
- Equivalent Circuit of the Membrane
 - What Gives Rise to C, R, and V?
 - Model of the Resting Membrane
 - Passive Electrical Properties
 - Time Constant and Length Constant
 - Effects on Synaptic Integration
 - □ Voltage-Clamp Analysis of the Action Potential



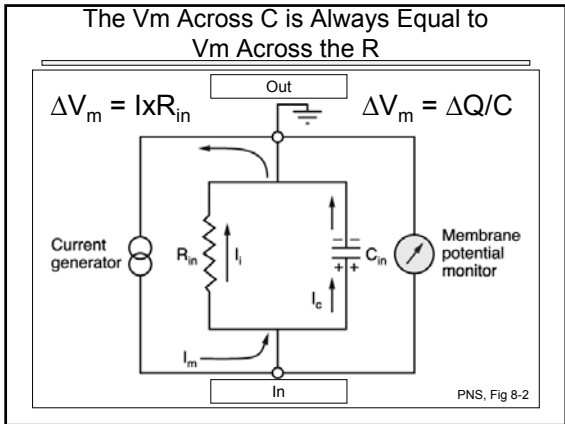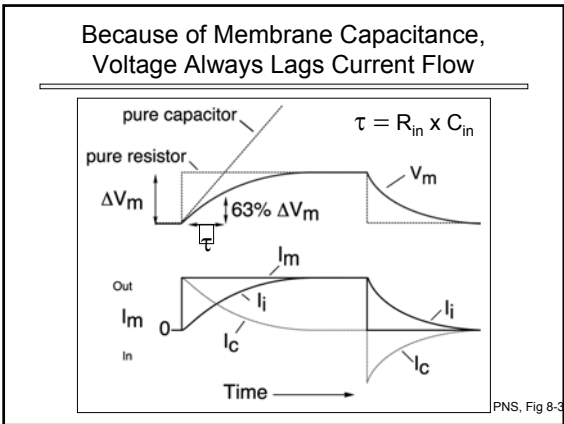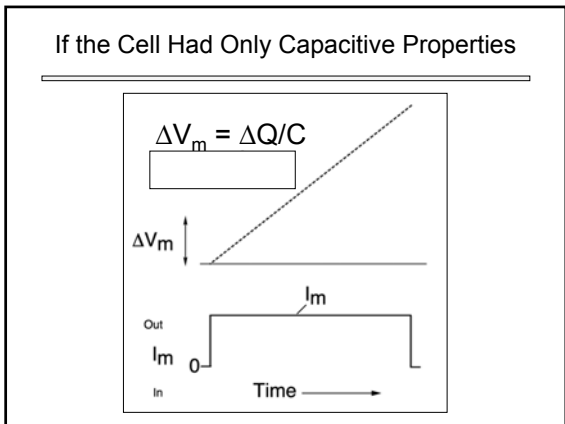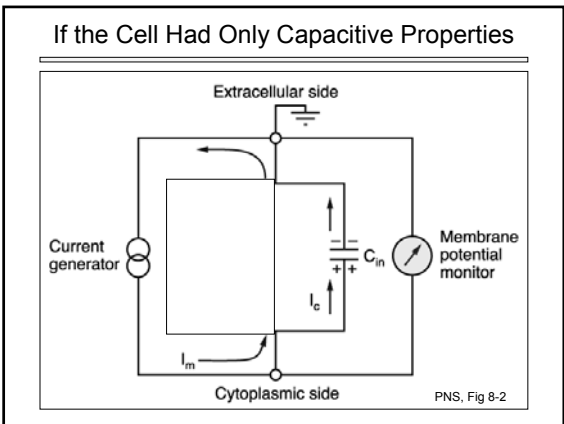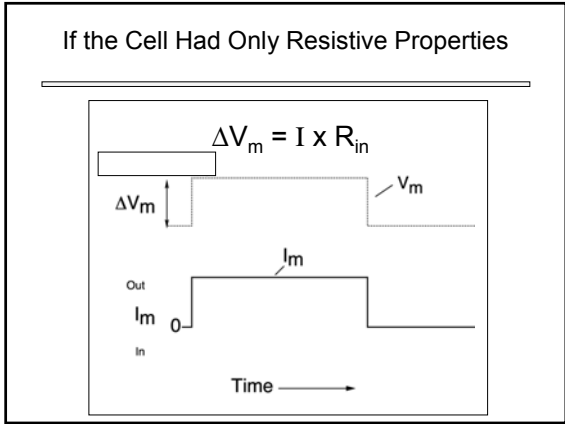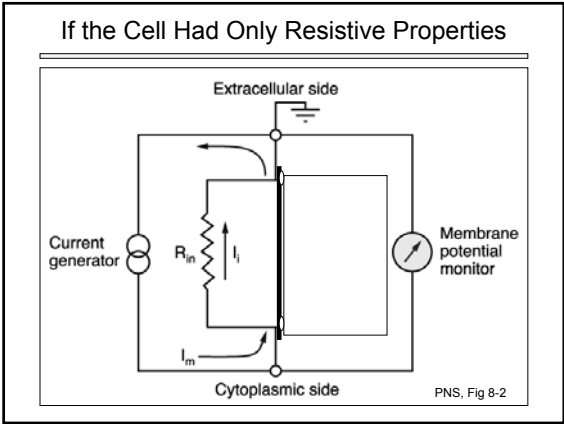


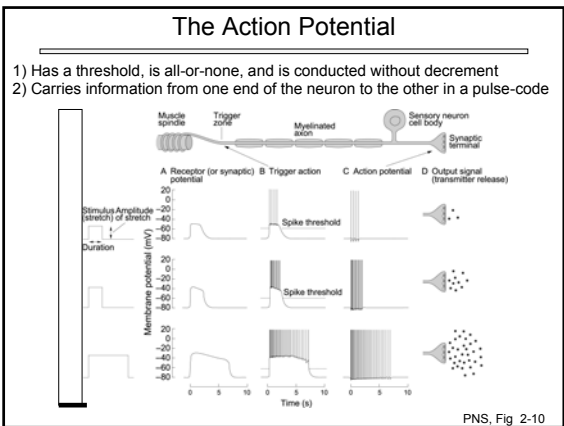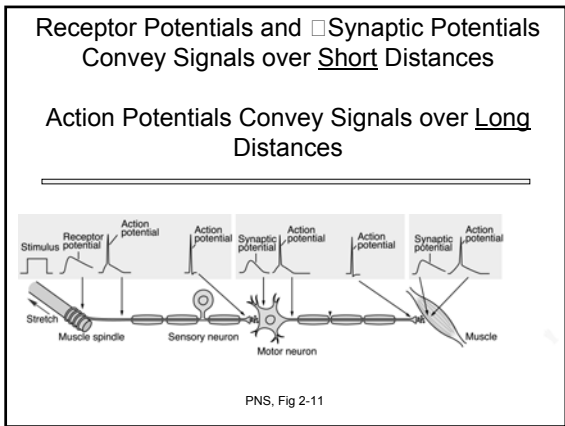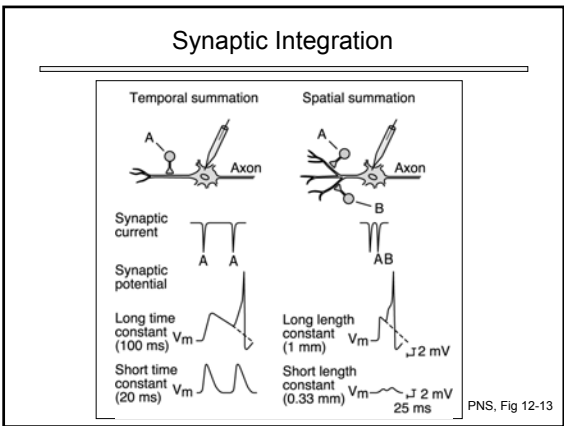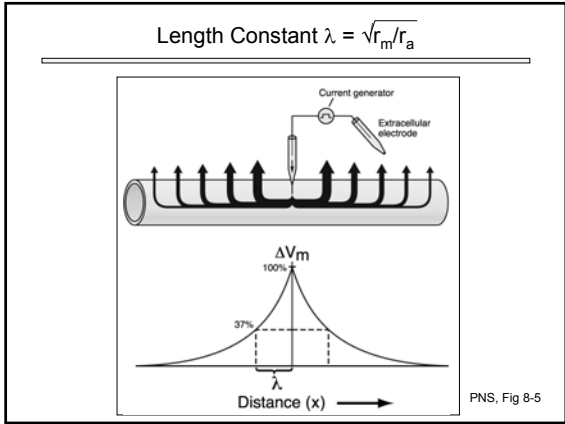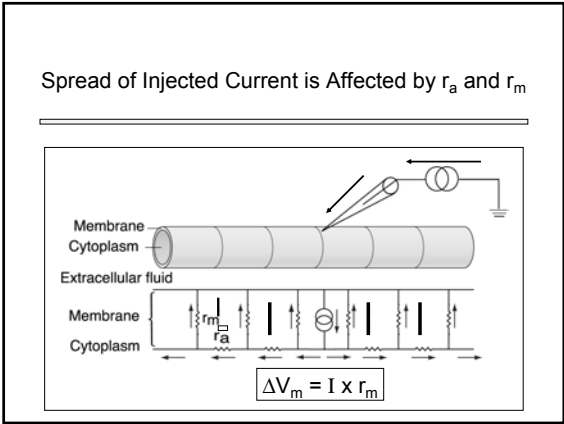

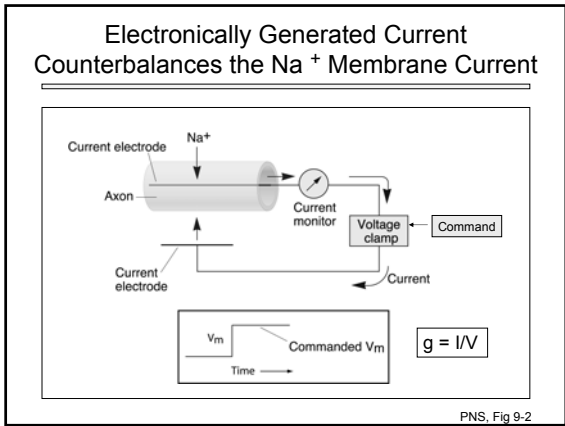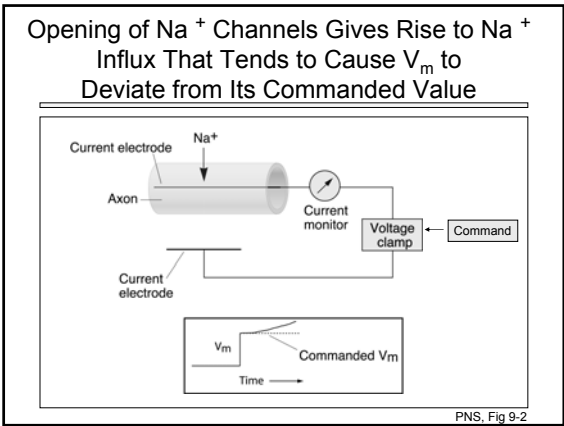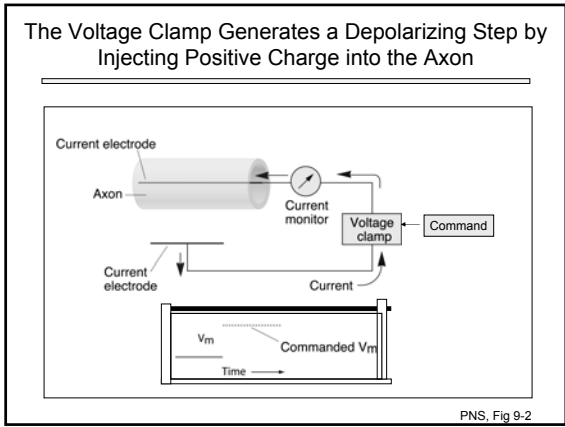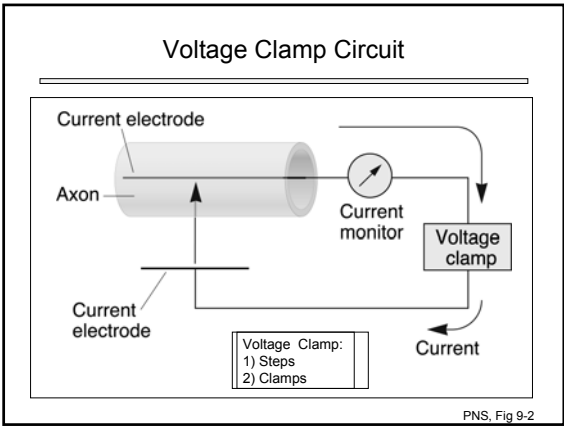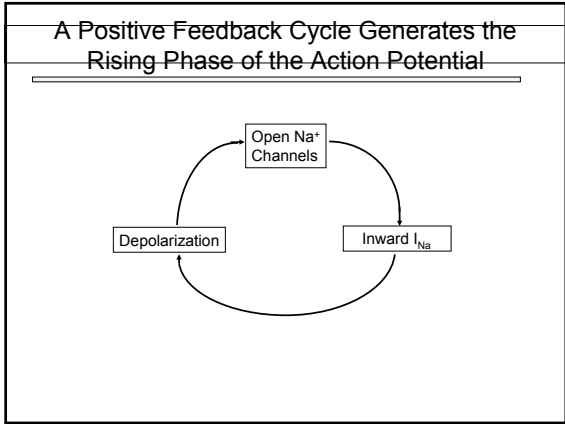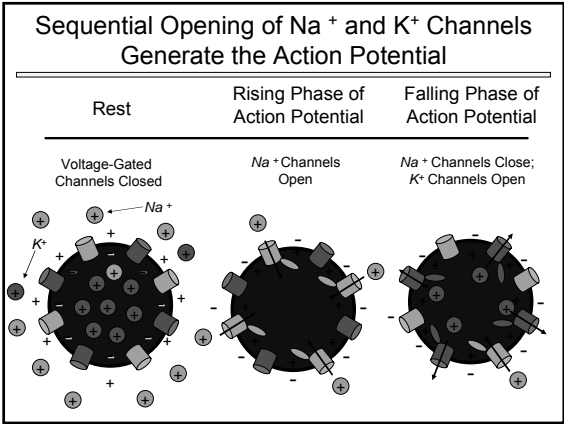- Equivalent Circuit of the Membrane and Passive Electrical Properties
- Equivalent Circuit of the Membrane
 - What Gives Rise to C, R, and V?
 - Model of the Resting Membrane
 - Passive Electrical Properties
 - Time Constant and Length Constant
 - Effects on Synaptic Integration
 - Voltage-Clamp Analysis of the Action Potential



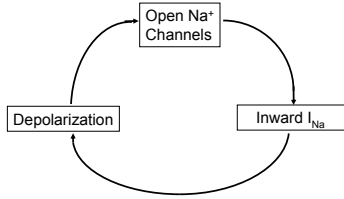Where Does the Voltage Clamp Interrupt the Positive Feedback Cycle?



The Voltage Clamp Interrupts the Positive Feedback Cycle Here

