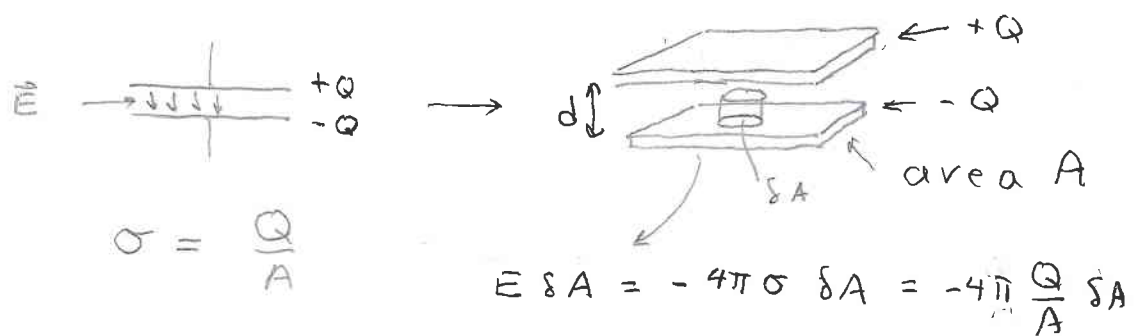


4. Parallel plate capacitor



$$\sigma = \frac{Q}{A}$$

$$E \delta A = -4\pi\sigma \delta A = -4\pi \frac{Q}{A} \delta A$$

$$\phi_{top} - \phi_{bot} = V = -E \cdot d = \frac{4\pi Q}{A} d$$

$$\text{or } V = \frac{1}{C} Q \quad \rightarrow \quad C = \frac{A}{4\pi d}$$

5. Units

for esu $C = \frac{Q}{V} \sim \text{cm}$

for SI $C = \frac{Q}{V} \sim \frac{\text{coulomb}}{\text{volt}}$

1 Farad = $\frac{1 \text{ coulomb}}{1 \text{ volt}} \equiv \text{Farad}$

$$= \frac{3 \times 10^9 \text{ esu}}{\frac{1}{300} \text{ stat-volt}} = 9 \times 10^{11} \text{ cm}$$

↑
(2.99792458)²

a Farad is a large unit

a cm " " small unit

6. Energy stored in a capacitor




move δQ from lower to upper conductor

$$\delta W = V \delta Q = \frac{Q}{C} \delta Q$$

$$E = \int_0^E \delta W = \int_0^Q \frac{Q}{C} dQ = \frac{Q^2}{2C}$$

Check for case of // plate capacitor

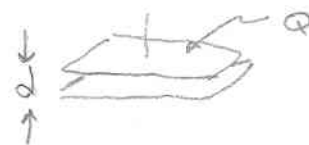


$$C = \frac{A}{4\pi d} \quad \& \quad E = \frac{4\pi d}{2A} Q^2$$


or $E = \underbrace{Ad}_{\text{volume}} \underbrace{\frac{|\vec{E}|^2}{8\pi}}_{\text{energy density}}$ $E = 4\pi Q/A$

$$= Ad \frac{(4\pi Q/A)^2}{8\pi} = 2\pi \frac{dQ^2}{A} \checkmark$$

7. Combine capacitors

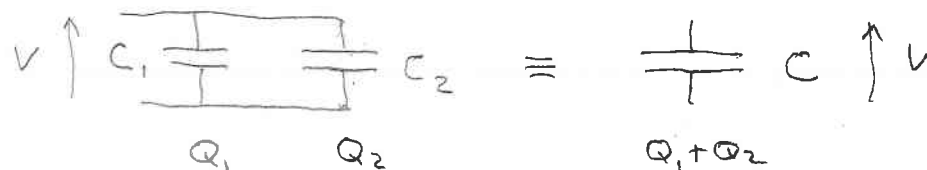

6. Energy stored in a capacitor

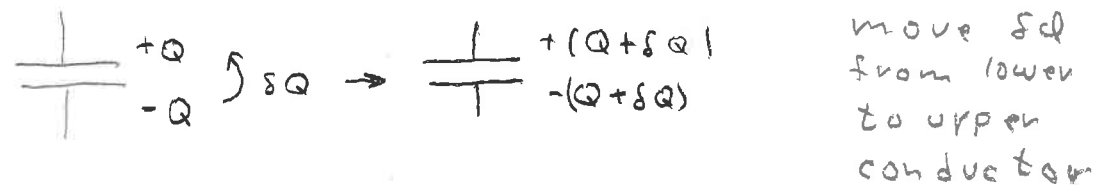

$$\delta W = V \delta Q = \frac{Q}{C} \delta Q$$

$$E = \int_0^Q \delta W = \int_0^Q \frac{Q}{C} dQ = \frac{Q^2}{2C}$$

Check for case of // plate capacitor




$$C = \frac{A}{4\pi d} \quad \& \quad E = \frac{4\pi d}{2A} Q^2$$

or $E = \underbrace{Ad}_{\text{volume}} \frac{|\vec{E}|^2}{8\pi}$ $E = 4\pi Q/A$
energy density

$$= Ad \frac{(4\pi Q/A)^2}{8\pi} = 2\pi \frac{dQ^2}{A} \checkmark$$


7. Combine capacitors

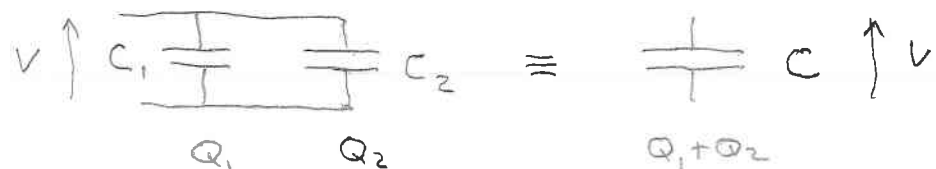

$$Q_1 = C_1 V, \quad Q_2 = C_2 V$$

$$\text{So } Q = Q_1 + Q_2 = \frac{(C_1 + C_2)V}{C}$$

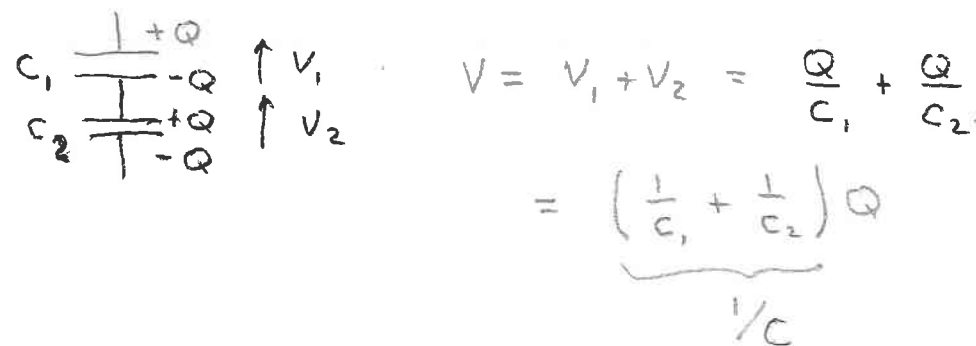
When two capacitor are joined in parallel $C = C_1 + C_2$




$$\text{so } C = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} = \frac{C_1 C_2}{C_1 + C_2}$$

Easy to generalize to the case of N capacitors:

parallel $C = \sum_{i=1}^N C_i$

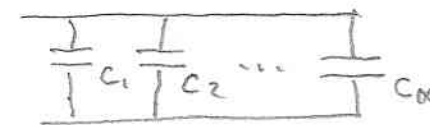

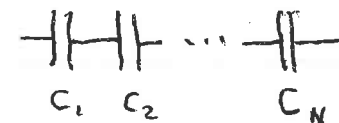
series: $C = \frac{1}{\sum_{i=1}^N \frac{1}{C_i}}$



$$Q_1 = C_1 V, \quad Q_2 = C_2 V$$



$$\text{So } Q = Q_1 + Q_2 = \underbrace{(C_1 + C_2)}_C V$$

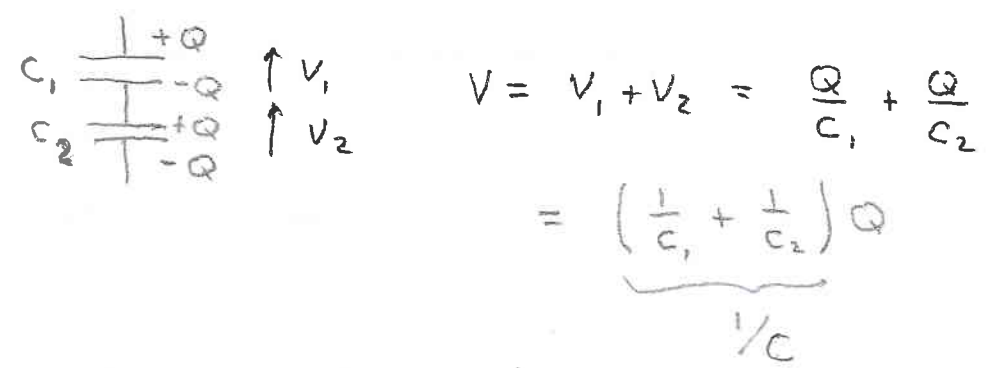When two capacitors are joined in parallel $C = C_1 + C_2$




$$\text{so } C = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} = \frac{C_1 C_2}{C_1 + C_2}$$

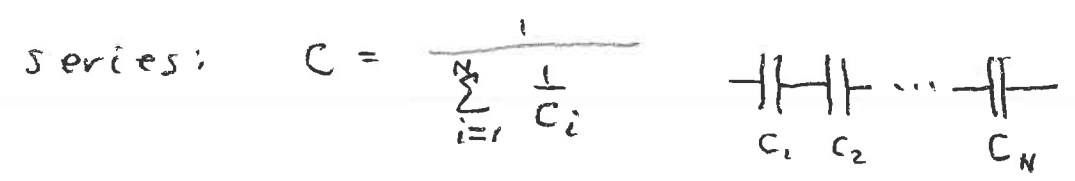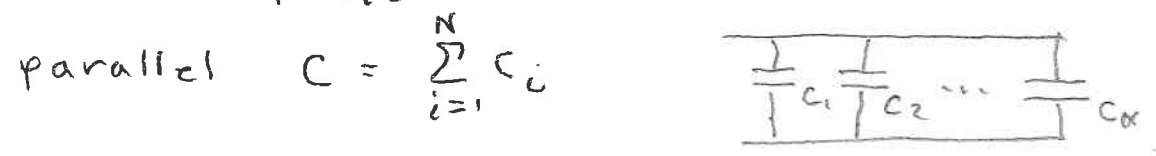Easy to generalize to the case of N capacitors:



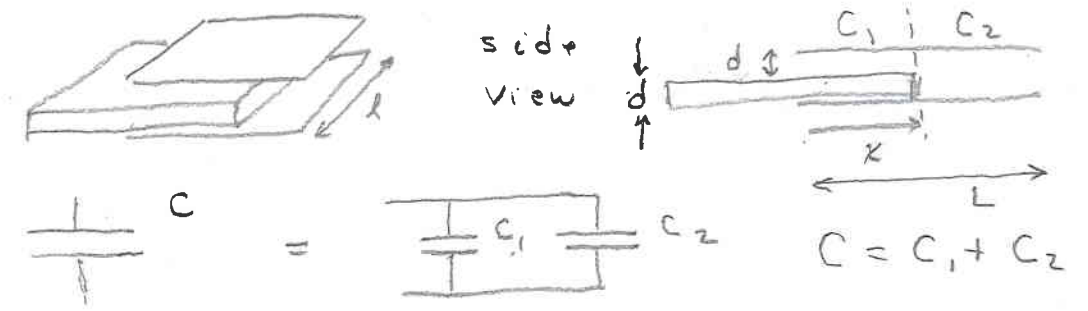8. Problem. Find force on conductor sliding inside a parallel-plate capacitor



$$C_1(x) = \frac{x l}{4\pi d}$$

$$C_2(x) = \frac{(L-x) l}{4\pi \cdot 2d}$$

$$C(x) = C_1(x) + C_2(x) = \frac{l}{8\pi d} [2x + L - x]$$

$$= \frac{l}{8\pi d} [L + x]$$


$$U(x) = \frac{1}{2} \frac{Q^2}{C(x)} = \frac{1}{2} Q^2 \frac{8\pi d}{l} \frac{1}{L+x}$$

Inward force on conductor

$$F = - \frac{dU}{dx} = - \frac{4\pi d Q^2}{l} \frac{d}{dx} \frac{1}{L+x}$$

$$= \frac{4\pi d Q^2}{l(L+x)^2} \quad \text{slab pulled in}$$

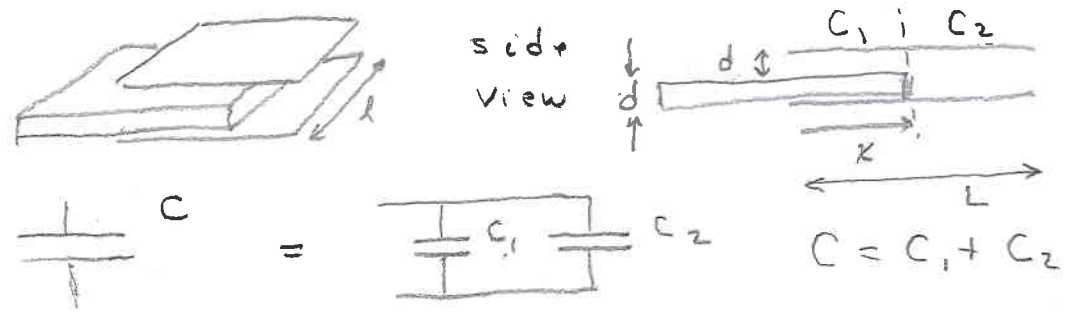8. Problem. Find force on conductor sliding inside a parallel-plate capacitor



$$C_1(x) = \frac{x l}{4\pi d} \quad C_2(x) = \frac{(L-x)l}{4\pi \cdot 2d}$$

$$C(x) = C_1(x) + C_2(x) = \frac{l}{8\pi d} [2x + L - x]$$

$$= \frac{l}{8\pi d} [L + x]$$

$$U(x) = \frac{1}{2} \frac{Q^2}{C(x)} = \frac{1}{2} Q^2 \frac{8\pi d}{l} \frac{1}{L+x}$$

Inward force on conductor

$$F = - \frac{dU}{dx} = - \frac{4\pi d Q^2}{l} \frac{d}{dx} \frac{1}{L+x}$$


$$= \frac{4\pi d Q^2}{l(L+x)^2} \quad \text{slab pulled in}$$

G Ohm's law and circuit theory

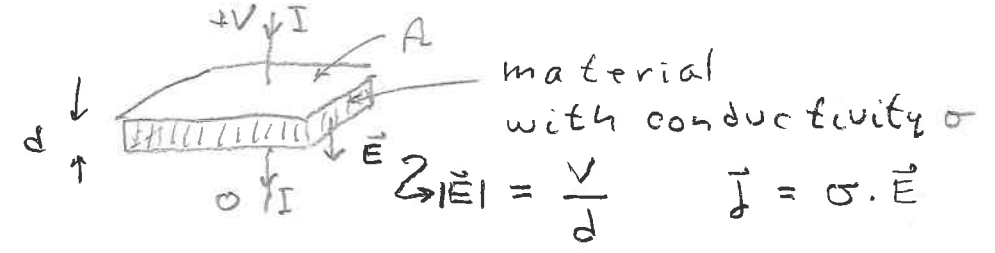1. Resistors Recall in our model

of conductivity $\vec{j} = \sigma \vec{E}$

where \vec{E} is the applied electric field, \vec{j} the resulting current density esu/cm²sec
 σ is the conductivity:



current $I = \int A = \sigma \frac{V}{d} A$

$$= \frac{V}{d/\sigma A} \equiv \frac{V}{R}$$

$V = IR$: Ohm's law $R = \frac{d}{\sigma A}$

Units esu: $\frac{\text{esu/cm}}{\text{esu/sec}} = \frac{\text{sec}}{\text{cm}}$

SI: $\frac{\text{Volt}}{\text{Amp}} \equiv \text{Ohm}$

$$= \frac{(1/300) \text{ stat volt}}{3 \times 10^9 \text{ esu/sec}}$$

Thus $\frac{\text{sec}}{\text{cm}} = 9 \times 10^{11} \text{ Ohm}$

impractically large


$$= \frac{1}{9 \times 10^{11}} \frac{\text{sec}}{\text{cm}}$$

G Ohm's law and circuit theory

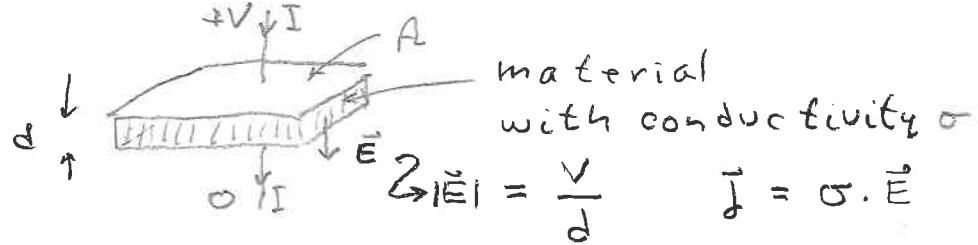1. Resistors Recall in our model

of conductivity $\vec{j} = \sigma \vec{E}$

where \vec{E} is the applied electric field, \vec{j} the resulting current density esu/cm²sec
 σ is the conductivity:



current $I = \int A = \sigma \frac{V}{d} A$

$$= \frac{V}{d/\sigma A} \equiv \frac{V}{R}$$

$V = IR$: Ohm's law $R = \frac{d}{\sigma A}$

Units

esu: $\frac{\text{esu/cm}}{\text{esu/sec}} = \frac{\text{sec}}{\text{cm}}$

SI: $\frac{\text{Volt}}{\text{Amp}} \equiv \text{Ohm}$

$$= \frac{(1/300) \text{ stat volt}}{3 \times 10^9 \text{ esu/sec}}$$

$$= \frac{1}{9 \times 10^{11}} \frac{\text{sec}}{\text{cm}}$$

Thus $\frac{\text{sec}}{\text{cm}} = 9 \times 10^{11} \text{ Ohm}$
 impractically large

2. Circuit theory

a) Introduce discrete elements with two terminal that can be connected with low (zero?) resistance wires


- easy to analyze
- join to create more general functions

two examples so far:

capacitor $Q = VC$

resistor $I = V/R$

b) Combine resistors

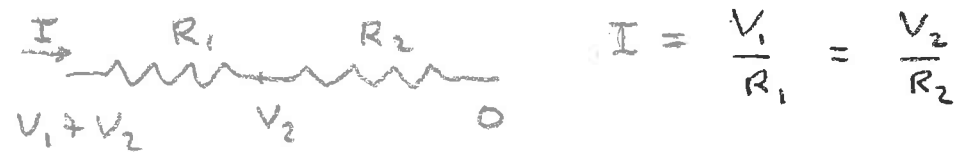

$\therefore V_1 + V_2 = (R_1 + R_2) I$

When combining resistors in series, add their resistances.

For N resistors in series $R = \sum_{i=1}^N R_i$


2. Circuit theory

a) Introduce discrete elements with two terminals that can be connected with low (zero?) resistance wires

- easy to analyze
- join to create more general functions

two examples so far:

capacitor  $Q = VC$

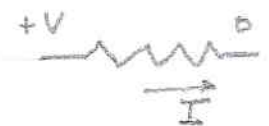resistor  $I = V/R$


b) Combine resistors

 $I = \frac{V_1}{R_1} = \frac{V_2}{R_2}$

$$\therefore V_1 + V_2 = (R_1 + R_2) I$$

When combining resistors in series, add their resistances.

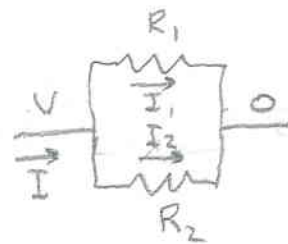For N resistors in series $R = \sum_{i=1}^N R_i$



$$I = I_1 + I_2 = \frac{V}{R_1} + \frac{V}{R_2}$$

$$= \left(\frac{1}{R_1} + \frac{1}{R_2} \right) V = \frac{V}{\frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}}$$


When combining two resistors in parallel, take the harmonic mean of their resistances:

$$R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$

For N resistors in parallel

$$R = \frac{1}{\sum_{i=1}^N \frac{1}{R_i}}$$


c) Combine $R + C$

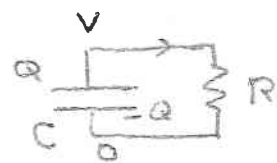

$$V = Q/C \quad I = V/R$$


$$I = - \frac{dQ}{dt}$$
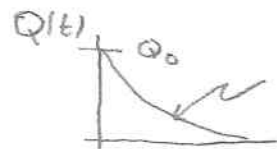
$$\therefore \frac{dQ}{dt} = - \frac{V}{R} = - \frac{Q}{RC} \quad \text{or } Q(t) = Q_0 e^{-\frac{t}{RC}}$$



an "RC" circuit

$\frac{t}{RC}$
cm sec/cm

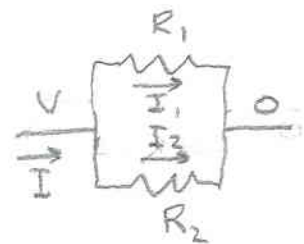

$$I = I_1 + I_2 = \frac{V}{R_1} + \frac{V}{R_2}$$

$$= \left(\frac{1}{R_1} + \frac{1}{R_2}\right)V = \frac{V}{\frac{1}{R_1} + \frac{1}{R_2}}$$


When combining two resistors in parallel, take the harmonic mean of their resistances:

$$R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$

For N resistors in parallel

$$R = \frac{1}{\sum_{i=1}^N \frac{1}{R_i}}$$

c) Combine R + C

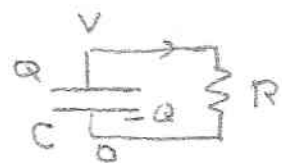

$$V = Q/C \quad I = V/R$$

$$I = - \frac{dQ}{dt}$$

$$\therefore \frac{dQ}{dt} = -\frac{V}{R} = -\frac{Q}{RC}$$

$$\text{or } Q(t) = Q_0 e^{-\frac{t}{RC}}$$

cm sec/cm




$$Q_0 e^{-t/RC}$$

$$Q(t=0) = Q_0$$

an "RC" circuit

d) Next add a battery

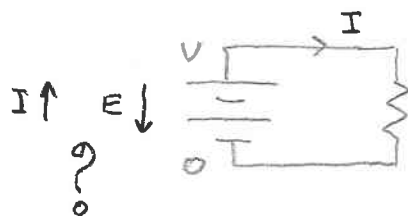


$V = IR$ Although current flows, V changes

only slowly, similar to a capacitor with huge capacitance. However, source of energy is chemical, not electrostatic.

- In a battery the charge moves in the direction opposite to the electric field
- Absurd since to excellent approximation only electrostatic forces are important.
- Need quantum mechanics!
- This magical source of current, driving ^{the} internal current against the internal electric field is called an electromotive force or EMF.

d) Next add a battery

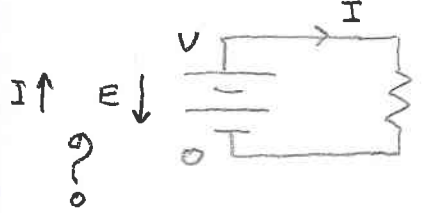

$V = IR$ Although


current flows, V changes

only slowly, similar to a capacitor with huge capacitance. However, source of energy is chemical, not electrostatic.

- In a battery the charge moves in the direction opposite to the electric field
- Absurd since to excellent approximation only electrostatic forces are important.
- Need quantum mechanics!
- This magical source of current, driving ^{the} internal current against the internal electric field is called an electromotive force or EMF.


Actually there are two sources of EMF:

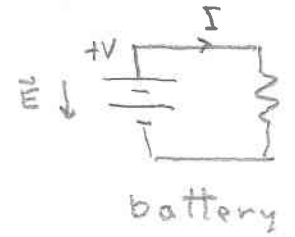- ① $\oint_C \vec{E} \cdot d\vec{r} = 0$ and charge is forced by quantum mechanics to move against the \vec{E} field




battery

or

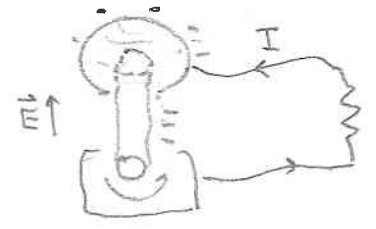

Van de Graaff generator

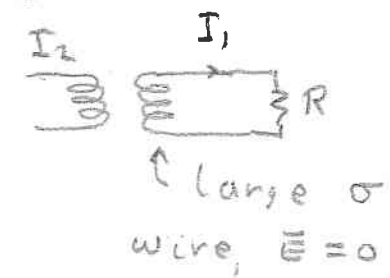- ② $\oint_C \vec{E} \cdot d\vec{r} = -\frac{1}{c} \frac{d\Phi_B}{dt}$ Faraday's law



$IR = EMF = M_{12} \frac{dI_2}{dt}$
 mutual inductance

We can now solve a multitude of problems with resistors, capacitors and batteries connected in interesting ways