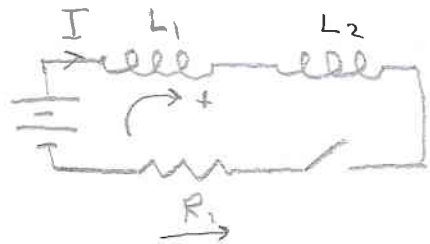


## 12. Combine inductors

(275)




$$\oint \vec{E} \cdot d\vec{l} = -\frac{1}{c} \frac{d\Phi}{dt}$$

$$= -\frac{1}{c} \frac{d\Phi_1}{dt} - \frac{1}{c} \frac{d\Phi_2}{dt}$$

$$-V + IR = -L_1 \frac{dI}{dt} - L_2 \frac{dI}{dt}$$

$$\text{or } V = IR + \underbrace{(L_1 + L_2)}_L \frac{dI}{dt}$$

Inductors in series add.

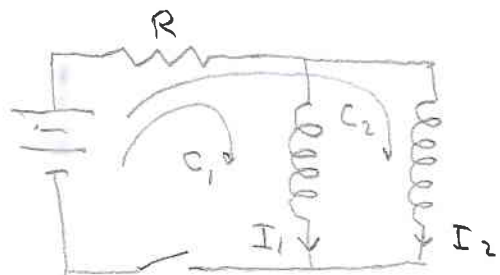

$$I = I_1 + I_2$$

$$\oint_{C_1} \vec{E} \cdot d\vec{r} = -L_1 \frac{dI_1}{dt}$$

$$-V + RI = -L_1 \frac{dI_1}{dt}$$

divide by  $L_1$

$$-V + RI = -L_2 \frac{dI_2}{dt}$$

divide by  $L_2$

add:

$$(-V + RI) \left( \frac{1}{L_1} + \frac{1}{L_2} \right) = -\frac{dI_1}{dt} - \frac{dI_2}{dt} = -\frac{dI}{dt}$$

$$V = RI + \frac{1}{\underbrace{\frac{1}{L_1} + \frac{1}{L_2}}_L} \frac{dI}{dt}$$

Inductors in parallel combine like resistors in parallel


## D. AC circuits 02/18/2021

(276)

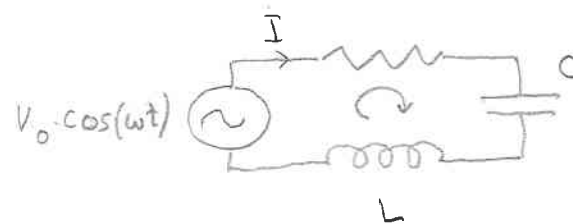1. Consider circuits driven by a simple oscillating voltage

$$V(t) = V_0 \cos \omega t$$

derive from  $\oint \vec{E} \cdot d\vec{l}$  an incident radio wave, ...



$$\oint \vec{E} \cdot d\vec{l} = -L \frac{dI}{dt}$$

$$-V_0 \cos \omega t + IR + \frac{Q}{C} = -L \frac{dI}{dt}$$

$$\text{or } L \frac{dI}{dt} + RI + \frac{Q}{C} = V_0 \cos \omega t$$

$$\text{or } L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = V_0 \cos \omega t$$

the same equation as forced S.H.M.


$$m \frac{d^2 x}{dt^2} + \sigma \frac{dx}{dt} + kx = F_0 \cos \omega t$$

easily solve by introducing a second equation

$$L \frac{d^2 Q_i}{dt^2} + R \frac{dQ_i}{dt} + \frac{1}{C} Q_i = V_0 \sin \omega t$$

## D. AC circuits

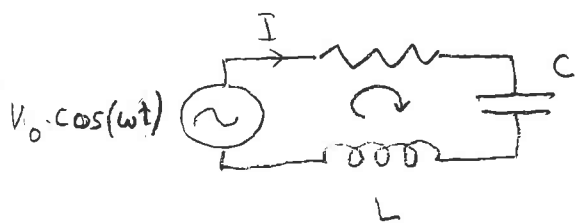1. Consider circuits driven by a simple oscillating voltage  $V(t) = V_0 \cos \omega t$ . Could derive from Con Ed an incident radio wave, ...



$$\oint \vec{E} \cdot d\vec{l} = -L \frac{dI}{dt}$$

$$-V_0 \cos \omega t + IR + \frac{Q}{C} = -L \frac{dI}{dt}$$

$$\text{or } L \frac{dI}{dt} + RI + \frac{Q}{C} = V_0 \cos \omega t$$

$$\text{or } L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = V_0 \cos \omega t$$

the same equation as forced S.H.M.

$$m \frac{d^2 x}{dt^2} + \sigma \frac{dx}{dt} + kx = F_0 \cos \omega t$$

easily solve by introducing a second equation

$$L \frac{d^2 Q_i}{dt^2} + R \frac{dQ_i}{dt} + \frac{1}{C} Q_i = V_0 \sin \omega t$$

Calling the solution to the first equation  $Q_r$ , multiplying the second equation by "i" & adding

$$L \frac{d^2}{dt^2} \underbrace{(Q_r + iQ_i)}_Q + R \frac{d}{dt} (Q_r + iQ_i) + \frac{1}{C} (Q_r + iQ_i) = V_0 (\cos \omega t + i \sin \omega t) = V_0 e^{i\omega t}$$

Thus, solve

$$L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{1}{C} Q = V_0 e^{i\omega t}$$

and find the real part of  $Q$ .

As in the case of the forced simple harmonic oscillator, this is easily solved by  $Q(t) = Q_0 e^{i\omega t}$

$$L (i\omega)^2 Q_0 e^{i\omega t} + R (i\omega) Q_0 e^{i\omega t} + \frac{1}{C} Q_0 e^{i\omega t} = V_0 e^{i\omega t}$$

we have a solution valid for all  $t$  if

$$L (i\omega)^2 Q_0 + R (i\omega) Q_0 + \frac{1}{C} Q_0 = V_0$$

Calling the solution to the first equation  $Q_r$ , multiplying the second equation by "i" & adding

$$L \frac{d^2}{dt^2} (\underbrace{Q_r + iQ_i}_Q) + R \frac{d}{dt} (Q_r + iQ_i) + \frac{1}{C} (Q_r + iQ_i) = V_0 (\cos \omega t + i \sin \omega t) e^{i\omega t}$$

Thus, solve

$$L \frac{d^2}{dt^2} Q + R \frac{d}{dt} Q + \frac{1}{C} Q = V_0 e^{i\omega t}$$

and find the real part of  $Q$ .

As in the case of the forced simple harmonic oscillator, this is easily solved by  $Q(t) = Q_0 e^{i\omega t}$

$$L (i\omega)^2 Q_0 e^{i\omega t} + R (i\omega) Q_0 e^{i\omega t} + \frac{1}{C} Q_0 e^{i\omega t} = V_0 e^{i\omega t}$$

we have a solution valid for all  $t$  if

$$L (i\omega)^2 Q_0 + R (i\omega) Q_0 + \frac{1}{C} Q_0 = V_0$$

However, it is more convenient & conventional to work with current

$$I(t) = \frac{dQ}{dt} = \frac{d}{dt} Q_0 e^{i\omega t} = \underbrace{i\omega Q_0}_{I_0} e^{i\omega t}$$

$$\text{so use } Q_0 = \frac{I_0}{i\omega}$$

$$i\omega L I_0 + R I_0 + \frac{1}{i\omega} I_0 = V_0$$

$$\text{or } I_0 = \frac{1}{i\omega L + R + \frac{1}{i\omega}} V_0$$

$$I_r(t) = \text{Re} \left\{ \frac{1}{i\omega L + R + \frac{1}{i\omega}} V_0 e^{i\omega t} \right\}$$

This is the steady state solution.

Recall we can also add any solution to the homogeneous equation

$$L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{1}{C} Q = 0$$

$$\text{solved by } Q(t) = e^{\lambda t}$$

$$[L \lambda^2 + R \lambda + \frac{1}{C}] e^{\lambda t} = 0$$

However, it is more convenient & conventional to work with current

$$I(t) = \frac{dQ}{dt} = \frac{d}{dt} Q_0 e^{i\omega t} = \underbrace{i\omega Q_0}_{I_0} e^{i\omega t}$$

so use  $Q_0 = \frac{I_0}{i\omega}$

$$i\omega L I_0 + R I_0 + \frac{C}{i\omega} I_0 = V_0$$

or  $I_0 = \frac{1}{i\omega L + R + \frac{C}{i\omega}} V_0$

$$I_r(t) = \text{Re} \left\{ \frac{1}{i\omega L + R + \frac{C}{i\omega}} V_0 e^{i\omega t} \right\}$$

This is the steady state solution.

Recall we can also add any solution to the homogeneous equation

$$L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{1}{C} Q = 0$$

solved by  $Q(t) = e^{\lambda t}$

$$[L\lambda^2 + R\lambda + \frac{1}{C}] e^{\lambda t} = 0$$

or  $\lambda^2 + \frac{R}{L}\lambda + \frac{1}{LC} = 0$

and  $\lambda = \frac{-\frac{R}{L} \pm \sqrt{(\frac{R}{L})^2 - \frac{4}{LC}}}{2}$

If  $\frac{R}{2L} < \frac{1}{LC}$ , underdamped

Use  $\omega_1 = \sqrt{\frac{1}{LC} - (\frac{R}{2L})^2}$  and

$$I(t) = \underbrace{\text{Re} \left\{ \frac{e^{i\omega t}}{i\omega L + R + \frac{1}{i\omega C}} V_0 \right\}}_{\text{steady-state}} + \underbrace{A e^{-\frac{R}{L}t} \cos(\omega_1 t + \phi)}_{\text{transient}}$$

choose  $A$  &  $\phi$  to obey initial conditions

We will usually work at large time and drop the transient solution  $e^{-t \frac{R}{L}} \rightarrow 0$

2. Interpret the math as a complex version of Ohm's law

$$I_0 = \frac{V_0}{i\omega L + R + \frac{1}{i\omega C}}$$

or  $\lambda^2 + \frac{R}{L}\lambda + \frac{1}{LC} = 0$

and  $\lambda = \frac{-\frac{R}{L} \pm \sqrt{(\frac{R}{L})^2 - \frac{4}{LC}}}{2}$

If  $\frac{R}{2L} < \frac{1}{LC}$ , under damped

Use  $\omega_1 = \sqrt{\frac{1}{LC} - (\frac{R}{2L})^2}$  and

$I(t) = \underbrace{\text{Re} \left\{ \frac{e^{i\omega t}}{i\omega L + R + \frac{1}{i\omega C}} V_0 \right\}}_{\text{steady-state}} + \underbrace{A e^{-\frac{R}{L}t} \cos(\omega_1 t + \phi)}_{\text{transient}}$

choose A & φ to obey initial conditions


We will usually work at large time and drop the transient solution  $e^{-t \frac{R}{L}} \rightarrow 0$

2. Interpret the math as a complex version of Ohm's law

$I_0 = \frac{V_0}{i\omega L + R + \frac{1}{i\omega C}}$

Replace

resistance R → impedance Z

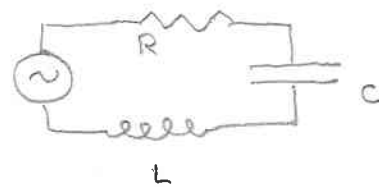

$Z = Z_L + Z_R + Z_C$

$Z_L = i\omega L, Z_R = R, Z_C = \frac{1}{i\omega C}$

Now look at steady-state solution:


$I(t) = \text{Re} \left\{ \frac{V_0 e^{i\omega t}}{i\omega L + R + \frac{1}{i\omega C}} \right\}$

$i\omega L + R + \frac{1}{i\omega C} = |i\omega L + R - \frac{i}{\omega C}| e^{i\phi}$

where  $\tan \phi = \frac{\omega L - \frac{1}{\omega C}}{R}$

$|i\omega L - \frac{i}{\omega C} + R| = \sqrt{(\omega L - \frac{1}{\omega C})^2 + R^2}$

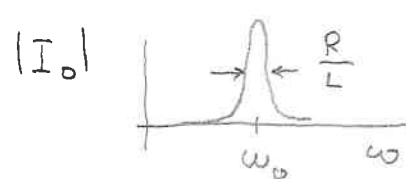$I(t) = \frac{V_0}{\sqrt{(\omega L - \frac{1}{\omega C})^2 + R^2}} \cos(\omega t - \phi)$




$\omega_0 L - \frac{1}{\omega_0 C} = 0$

$\omega_0 = \frac{1}{\sqrt{LC}}$

$(\omega L - \frac{1}{\omega C})^2 + R^2 = L^2 \left[ (\omega - \omega_0)^2 + \left(\frac{R}{L}\right)^2 \right]$

Replace

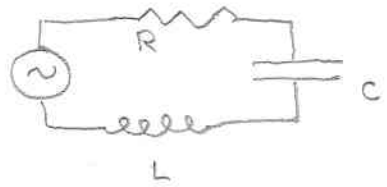resistance  $R \rightarrow$  impedance  $Z$



$$Z = Z_L + Z_R + Z_C$$

$$Z_L = i\omega L, Z_R = R, Z_C = \frac{1}{i\omega C}$$

Now look at steady-state solution:


$$I(t) = \text{Re} \left\{ \frac{V_0 e^{i\omega t}}{i\omega L + R + \frac{1}{i\omega C}} \right\}$$

$$i\omega L + R + \frac{1}{i\omega C} = |i\omega L + R - \frac{i}{\omega C}| e^{i\phi}$$

$$\text{where } \tan \phi = \frac{\omega L - \frac{1}{\omega C}}{R}$$

$$|i\omega L - \frac{i}{\omega C} + R| = \sqrt{(\omega L - \frac{1}{\omega C})^2 + R^2}$$
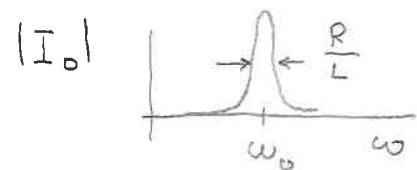
$$I(t) = \frac{V_0}{\sqrt{(\omega L - \frac{1}{\omega C})^2 + R^2}} \cos(\omega t - \phi)$$



$$\omega_0 L - \frac{1}{\omega_0 C} = 0$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$


$$(\omega L - \frac{1}{\omega C})^2 + R^2 = L^2 \left[ (\omega - \omega_0)^2 + \left(\frac{R}{L}\right)^2 \right]$$

Such a resonant circuit is at the heart of a radio receiver

- tuning  $\omega_0$  will choose the frequency which produces the largest  $I$
- as  $R \rightarrow 0$  this response becomes stronger & the selectivity (width of peak) becomes sharper

Describe how  $I$  depends on  $Z$ :
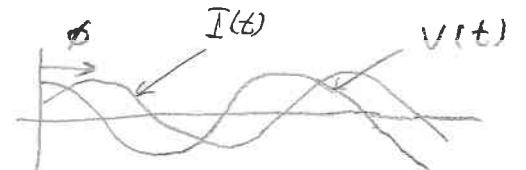
$$Z = i\omega L + R - \frac{i}{\omega C}$$




- Large  $\phi > 0$  current lags voltage
- Large  $\phi = 0$  current & voltage in phase
- $\frac{1}{C}$  large  $\phi < 0$  current leads voltage

Such a resonant circuit is at the heart of a radio receiver

- tuning  $\omega_0$  will choose the frequency which produces the largest  $I$
- as  $R \rightarrow 0$  this response becomes stronger & the selectivity (width of peak) becomes sharper

Describe how  $I$  depends on  $Z$ :
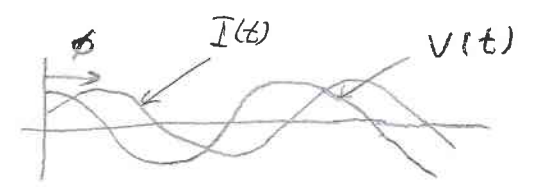
$$Z = i\omega L + R - \frac{i}{\omega C}$$



- a)  $L$  large  $\phi > 0$  current lags voltage
- b)  $R$  large  $\phi = 0$  current & voltage in phase
- c)  $\frac{1}{C}$  large  $\phi < 0$  current leads voltage

This same strategy of writing Kirchhoff's laws for real charges:

$$\textcircled{1} \sum_{\text{closed loops}} V_i = 0 + \textcircled{2} \sum_{\text{entering node}} I_i = 0$$

with real currents and "voltages"


$$V_r = V_i \cos(\omega t + \phi_i) \text{ or } V_r = L \frac{d^2 Q_r}{dt^2}$$

$$\text{or } V_r = R \frac{dQ_r}{dt} \text{ or } V_r = \frac{1}{C} Q_r$$

adding imaginary currents & voltages with  $Q_r \rightarrow iQ_i$  &  $V_i \cos(\omega t + \phi) \rightarrow iV_i \sin(\omega t + \phi)$

dividing type  $\textcircled{1}$  equations by  $i\omega$  and adding will give complex Kirchhoff laws with  $R_i \rightarrow Z_i$  if we hypothesize  $Q_r + iQ_i = Q_0 e^{i\omega t}$  for each case.

3. Example:

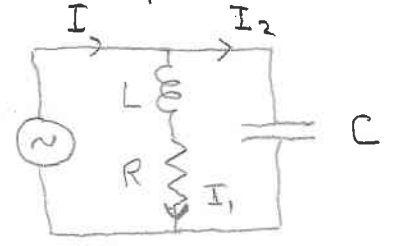

$$Z = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2}}$$

$$= \frac{1}{i\omega L + R + i\omega C}$$

This same strategy of writing Kirchhoff's laws for real charges:

$$\textcircled{1} \sum_{\text{closed loops}} V_i = 0 + \textcircled{2} \sum_{\text{entering node}} I_i = 0$$

with real currents and "voltages"


$$V_r = V_0 \cos(\omega t + \phi_i) \text{ or } V_r = L \frac{d^2 Q_r}{dt^2}$$

$$\text{or } V_r = R \frac{dQ_r}{dt} \text{ or } V = \frac{1}{C} Q_r$$

adding imaginary currents + voltages with  $Q_r \rightarrow iQ_i$  &  $V_0 \cos(\omega t + \phi) \rightarrow iV_0 \sin(\omega t + \phi)$

dividing type  $\textcircled{1}$  equations by  $i\omega$  and adding will give complex Kirchhoff laws with  $R_i \rightarrow Z_i$  if we hypothesize  $Q_r + iQ_i = Q_0 e^{i\omega t}$  for each case.

3. Example:

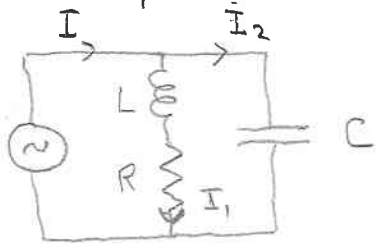

$$Z = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2}}$$

$$= \frac{1}{\frac{1}{i\omega L + R} + i\omega C}$$


$$Z = \frac{i\omega L + R}{1 + i\omega C(i\omega L + R)}$$

$$|I| = \left| \frac{V_0}{Z} \right| = |V_0| \left[ \frac{(1 - \omega^2 LC)^2 + \omega^2 R^2 C^2}{R^2 + \omega^2 L^2} \right]^{1/2}$$

for  $R \rightarrow 0$  &  $\omega \rightarrow \frac{1}{\sqrt{LC}}$   $Z \rightarrow \infty$

The oscillating LC circuit will exactly create applied voltage and no current flows into circuit. When  $R \neq 0$  current does flow to compensate power lost in  $R$ .


4. Discuss power in AC circuits

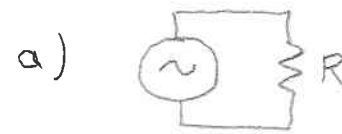

$$V = V_0 \cos \omega t$$

$$I = \frac{V_0}{R} \cos \omega t$$
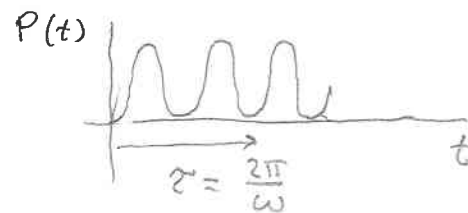
$$P(t) = V(t) I(t) = \frac{V_0^2}{R} \cos^2 \omega t$$



To calculate average power consumed integrate over one period

$$Z = \frac{i\omega L + R}{1 + i\omega C(i\omega L + R)}$$


(283)

$$|I| = \left| \frac{V_0}{Z} \right| = |V_0| \left[ \frac{(1 - \omega^2 LC)^2 + \omega^2 R^2 C^2}{R^2 + \omega^2 L^2} \right]^{1/2}$$

for  $R \rightarrow 0$  &  $\omega \rightarrow \frac{1}{\sqrt{LC}}$   $Z \rightarrow \infty$

The oscillating LC circuit will exactly create applied voltage and no current flows into circuit. When  $R \neq 0$  current does flow to compensate power lost in R.


4. Discuss power in AC circuits

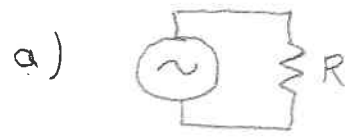

$$V = V_0 \cos \omega t$$

$$I = \frac{V_0}{R} \cos \omega t$$
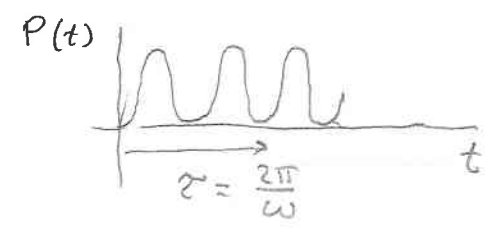
$$P(t) = V(t) I(t) = \frac{V_0^2}{R} \cos^2 \omega t$$



To calculate average power consumed integrate over one period

(284)

$$\bar{P} = \frac{1}{T} \frac{V_0^2}{R} \int_0^T \cos^2 \omega t dt$$

$$= \frac{1}{T} \frac{V_0^2}{R} \int_0^T \frac{1}{2} (\cos^2 \omega t + \sin^2 \omega t) dt$$

$$= \frac{1}{2} \frac{V_0^2}{R} = \frac{1}{2} V_0 I_0$$

note averaging over many cycles will give the same result.

To avoid the  $\frac{1}{2}$  factor AC current and voltage is usually give as the "root mean squared" value

$$V_{RMS} = \left[ \int_0^T V_0^2 \cos^2 \omega t dt \right]^{1/2} = \frac{1}{\sqrt{2}} V_0$$

the  $\bar{P} = V_{RMS} I_{RMS}$

For an average over a long time T with  $nT \leq T < (n+1)T$

$$\bar{P} = \frac{1}{T} \int_0^T V_0 I_0 \cos^2 \omega t dt$$

$$\approx \frac{1}{nT} \int_0^{nT} V_0 I_0 \cos^2 \omega t dt = \frac{1}{2} V_0 I_0$$